

# GATE ASSIGNMENT

Vooribindi Chandini  
 chandini.vooribindi@gmail.com  
 IITH - IITH-Future Wireless Communication

## CONTENTS

### I. QUESTION

- 1) Which one of the following options is CORRECT for the given logic circuit?
- (a)  $P = 1, Q = 1; X = 0$   
 (b)  $P = 1, Q = 0; X = 0$   
 (c)  $P = 0, Q = 1; X = 0$   
 (d)  $P = 0, Q = 0; X = 1$

### II. ANSWER

$$\rightarrow P' + Q$$

Therefore, the Boolean function  $F(X) = (P' + Q)$

### III. LOGIC DIAGRAM

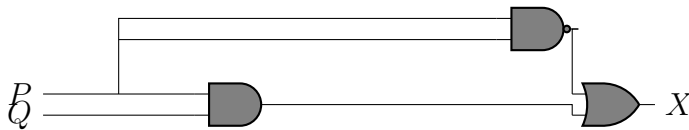


Fig. 1

### IV. TRUTH TABLE

$P$	$Q$	$P.Q$	$P'$	$X$
0	0	0	1	1
0	1	0	1	1
1	0	0	0	0
1	1	1	0	1

Truth table for Boolean Function  $X$

### V. K-MAP IMPLEMENTATION

Using the boolean logic output  $F$  can be expressed in terms of the inputs  $X, Y, Z$  with the help of the following Kmap.

	$P$	
	0	1
$Q$	0	1
	1	1

Fig. 2

### VI. COMPONENTS

Component	Values	Quantity
Arduino	UNO	1
LED		1
Resistor	220ohms	1
Jumper Wires	M-M	5
Breadboard		1

### VII. IMPLEMENTATION

Arduino PIN	INPUT	OUTPUT
2	P	
3	Q	
13		X

Connections

### Procedure

1. Connect the circuit as per the above table.
2. Connect inputs to Vcc for logic 1, ground for logic 0.
3. Execute the circuit using the below code.

<https://github.com/Chandinivooribindi/FWCgate/2023>

4. Change the values of P,Q in the code and verify the Truth Table.